



Faculty of Engineering and Technology

Department of Electrical and Computer Engineering

DIGITAL ELECTRONICS AND COMPUTER  
ORGANIZATION LABORATORY (ENCS2110)

**“Pre-Lab3”**

---

Prepared by:

Name: Eman Asfour



Number: 1200206


Instructor: Dr. Jamal Seyam


Section: 4


Date: 8 / 7 / 2023

Design a circuit which uses an SN74151 to implement a sum-of-products expression, as follows: a) Convert the following expression into summation form (i.e.,  $F(A, B, C) = \sum (...)$ ):  $Y = f(A, B, C) = A\bar{B} + \bar{B}C$  b) Sketch on Figure 3.1 the input connections necessary to implement the function in part (a). Observe that the inputs are connected to 0 or 1 depending on the value of the function for that min ter

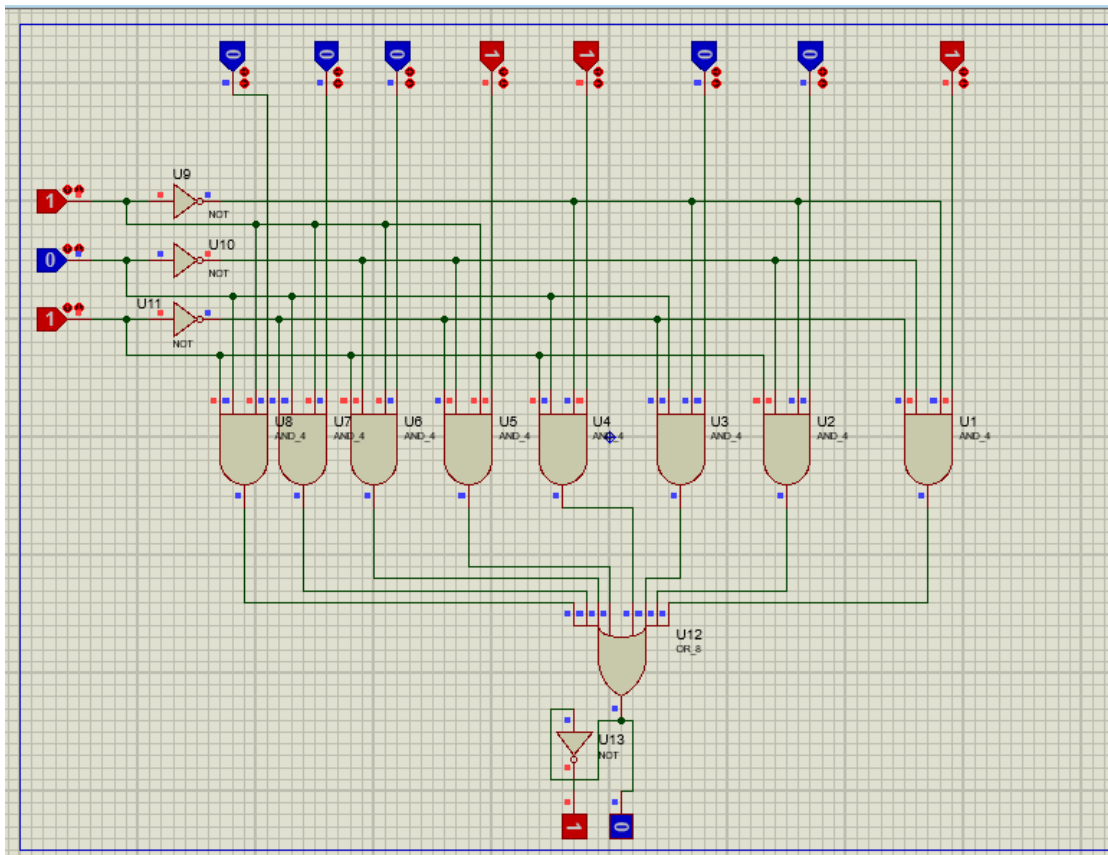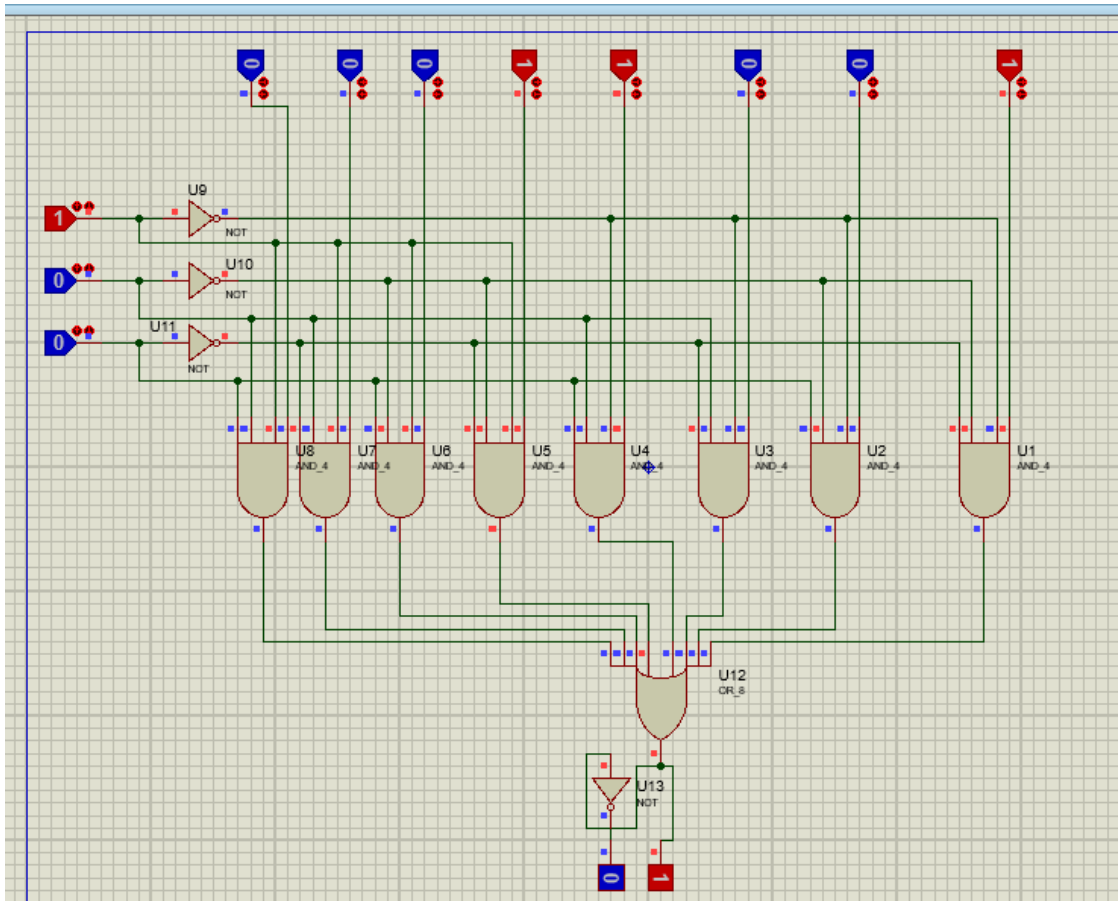

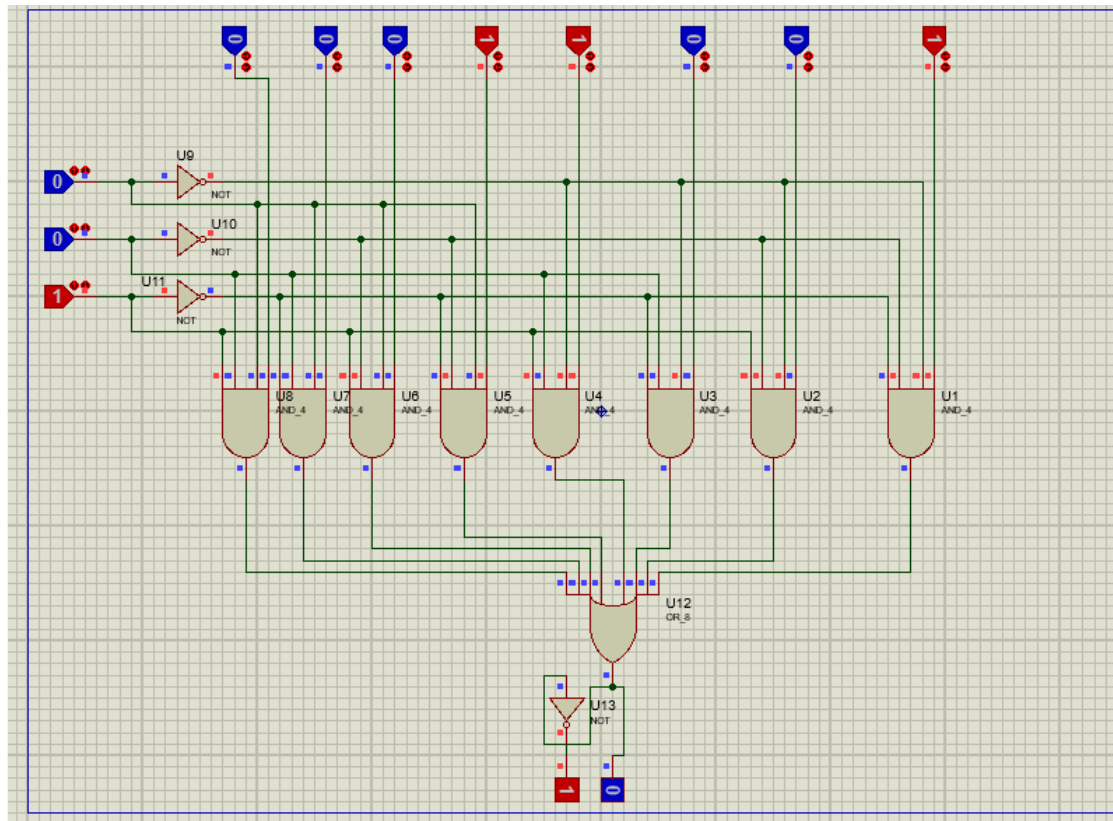


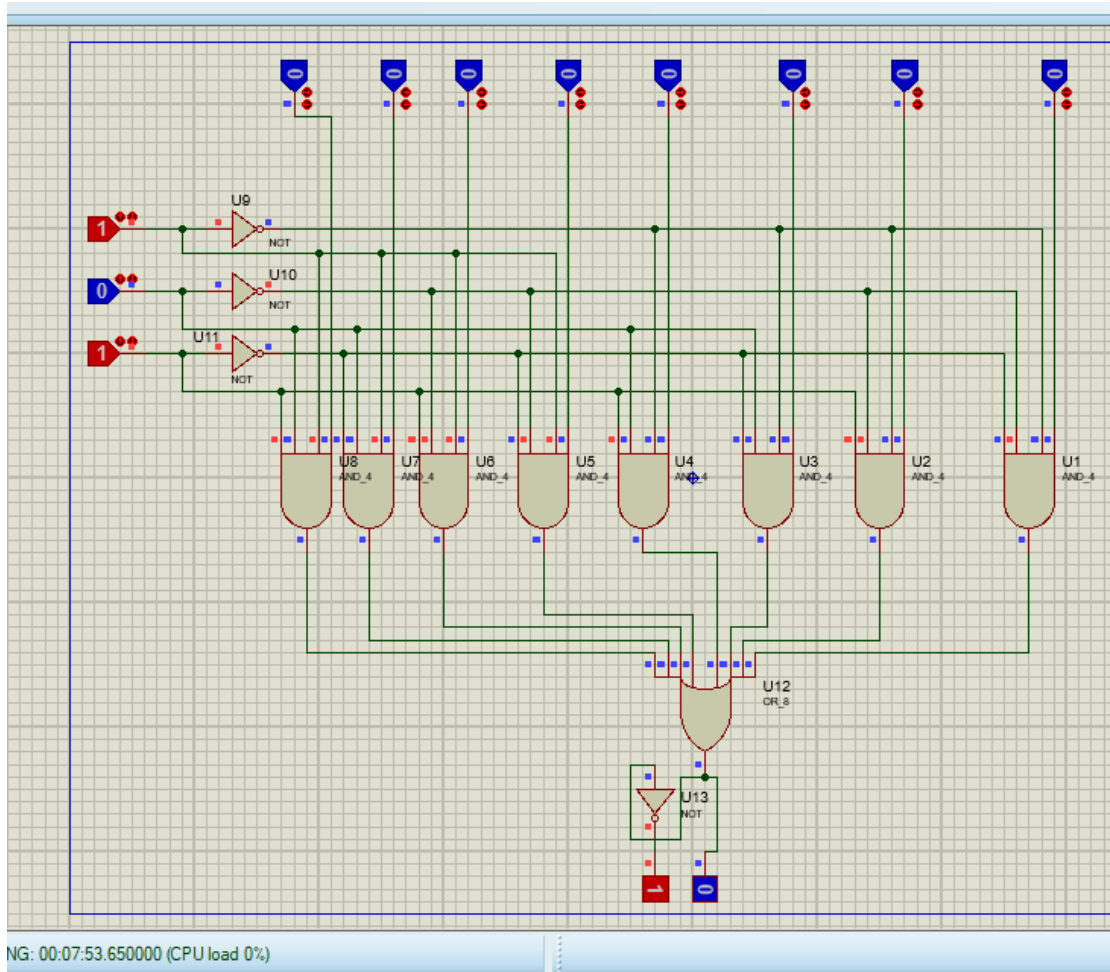


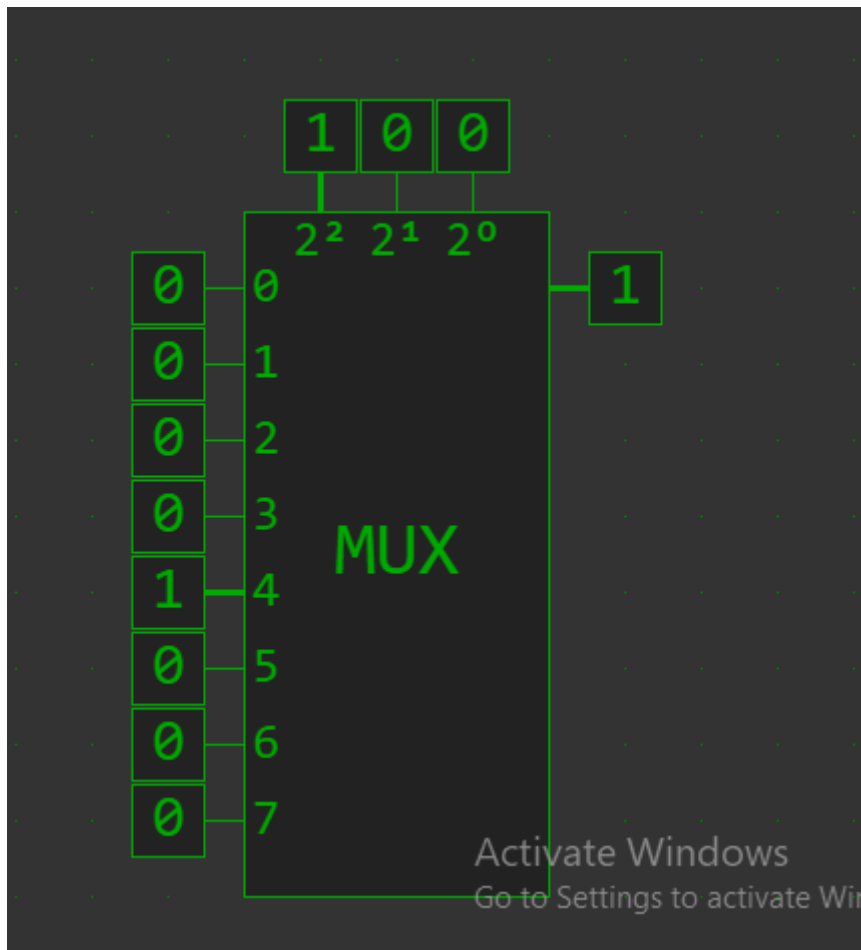

Select Data Inputs			Output
$S_2$	$S_1$	$S_0$	Y
0	0	0	$D_0$
0	0	1	$D_1$
0	1	0	$D_2$
0	1	1	$D_3$
1	0	0	$D_4$
1	0	1	$D_5$
1	1	0	$D_6$
1	1	1	$D_7$

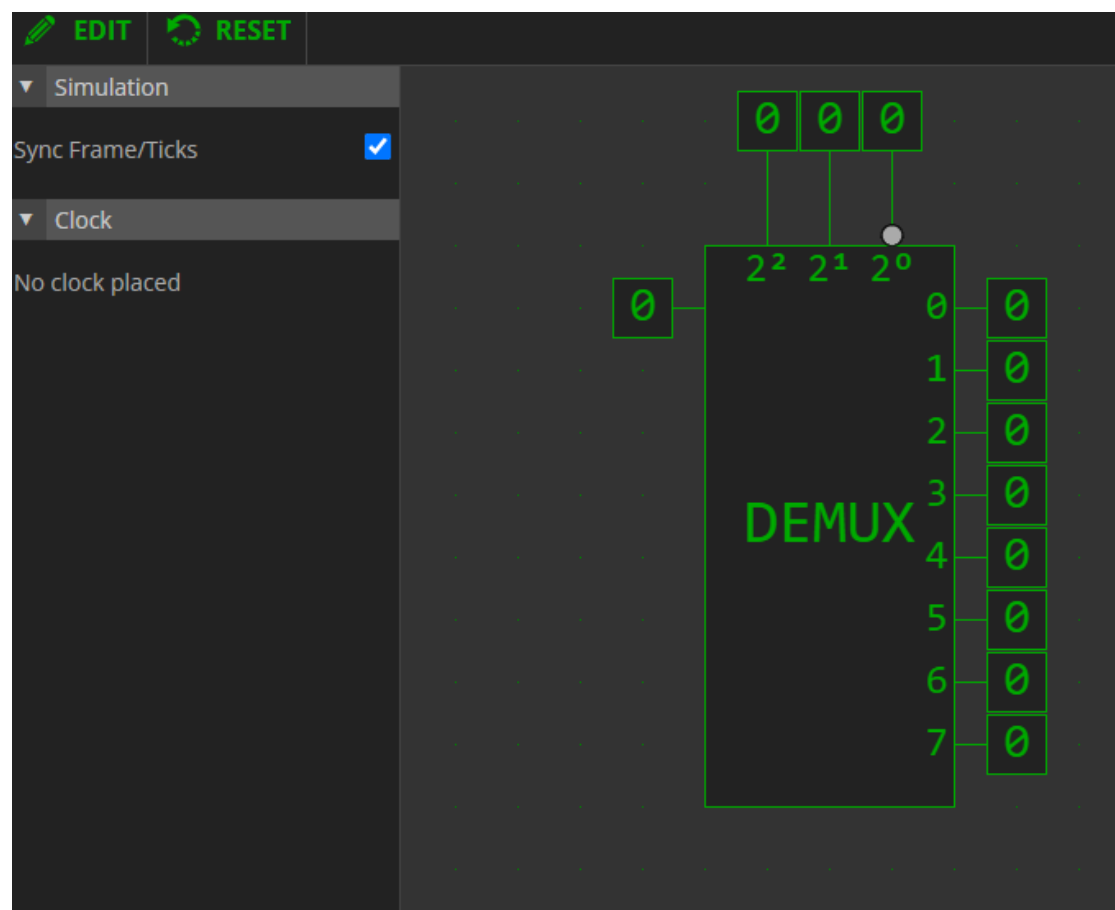Design a circuit which uses an SN74138 Demultiplexer to implement a sum-of-products expression, as follows: a) Convert the following expression into summation (Sum of Products –SOP-) form (i.e.  $F(A,B,C)=\sum(...)$ ):  $Y = f(A, B, C) = ABC + B\bar{C}$



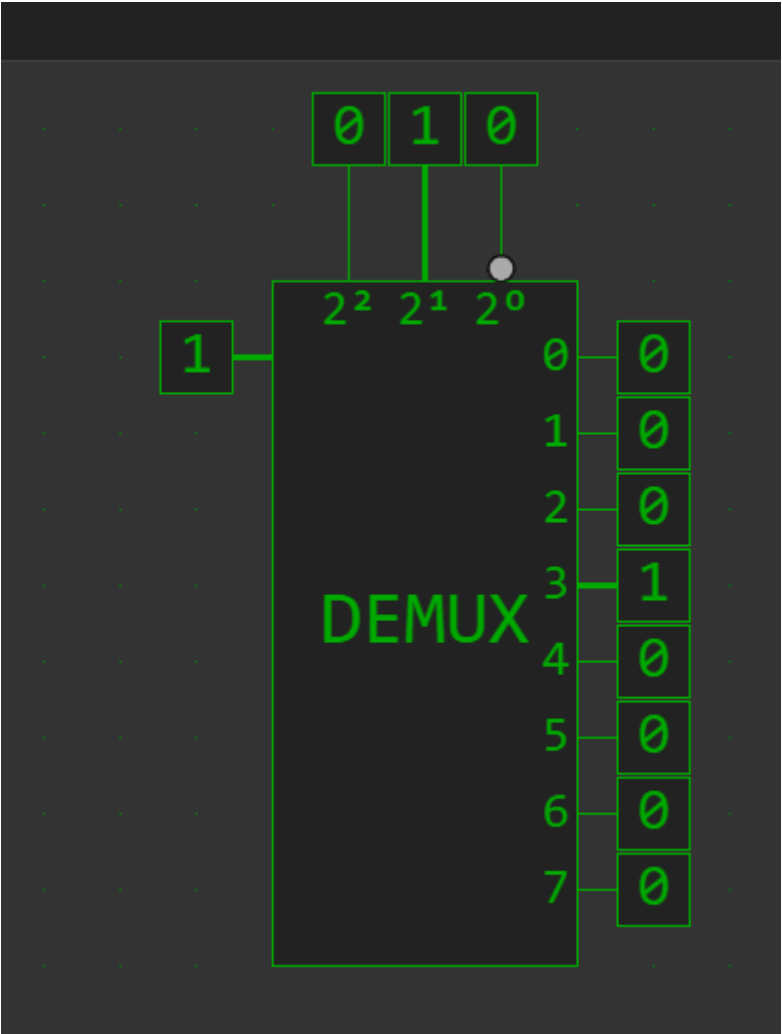

Example demultiplexer

INPUTS			Output							
S <sub>2</sub>	S <sub>1</sub>	S <sub>0</sub>	Y <sub>7</sub>	Y <sub>6</sub>	Y <sub>5</sub>	Y <sub>4</sub>	Y <sub>3</sub>	Y <sub>2</sub>	Y <sub>1</sub>	Y <sub>0</sub>
0	0	0	0	0	0	0	0	0	0	A
0	0	1	0	0	0	0	0	0	A	0
0	1	0	0	0	0	0	0	A	0	0
0	1	1	0	0	0	0	A	0	0	0
1	0	0	0	0	0	A	0	0	0	0
1	0	1	0	0	A	0	0	0	0	0
1	1	0	0	A	0	0	0	0	0	0
1	1	1	A	0	0	0	0	0	0	0



