



Faculty of Engineering and Technology

Department of Electrical and Computer Engineering

DIGITAL ELECTRONICS AND COMPUTER
ORGANIZATION LABORATORY (ENCS2110)

“Post-Lab 3 (Experiment3)”

Prepared by:

Name: Eman Asfour

Number: 1200206


Instructor: Dr. Jamal Seyam



Eng: Haleema Hmedan


Section: 4


Date: 8 / 13 / 2023

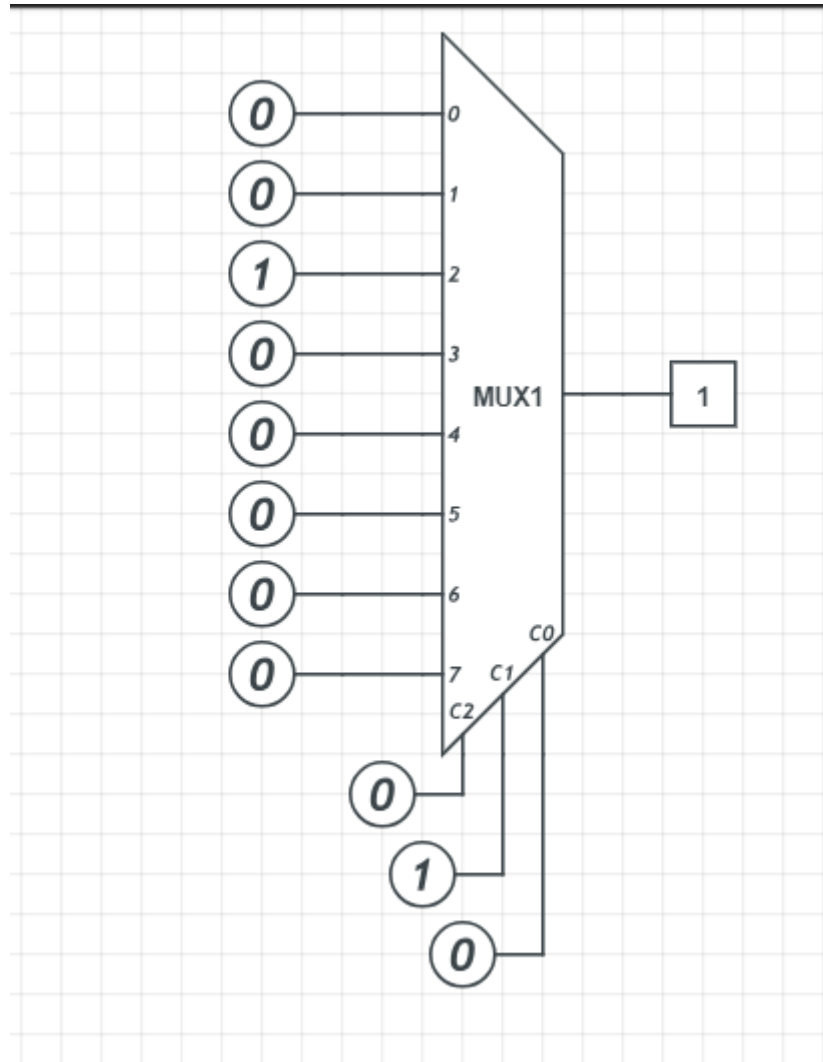1. Implement an 8x1 Multiplexer using lower order Multiplexers Show how to solve it.



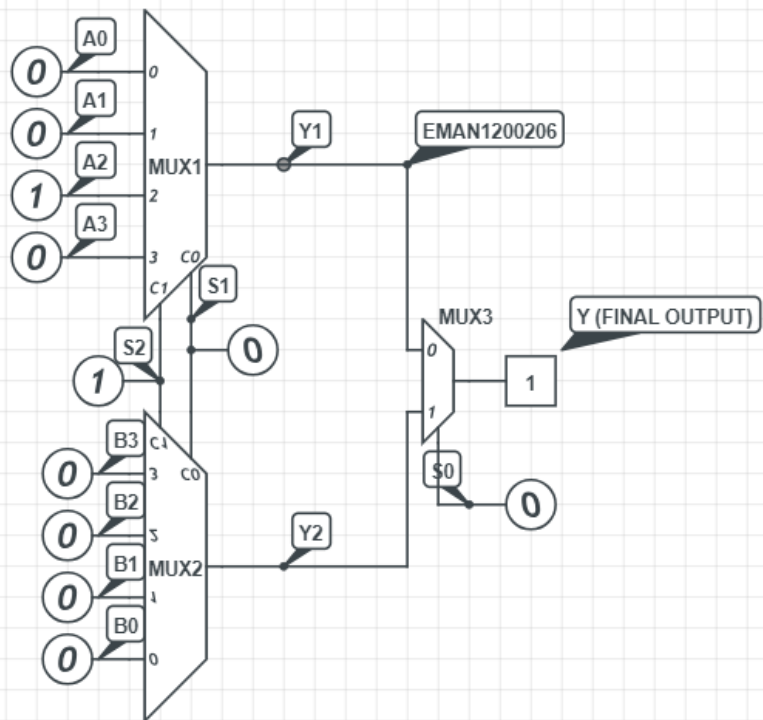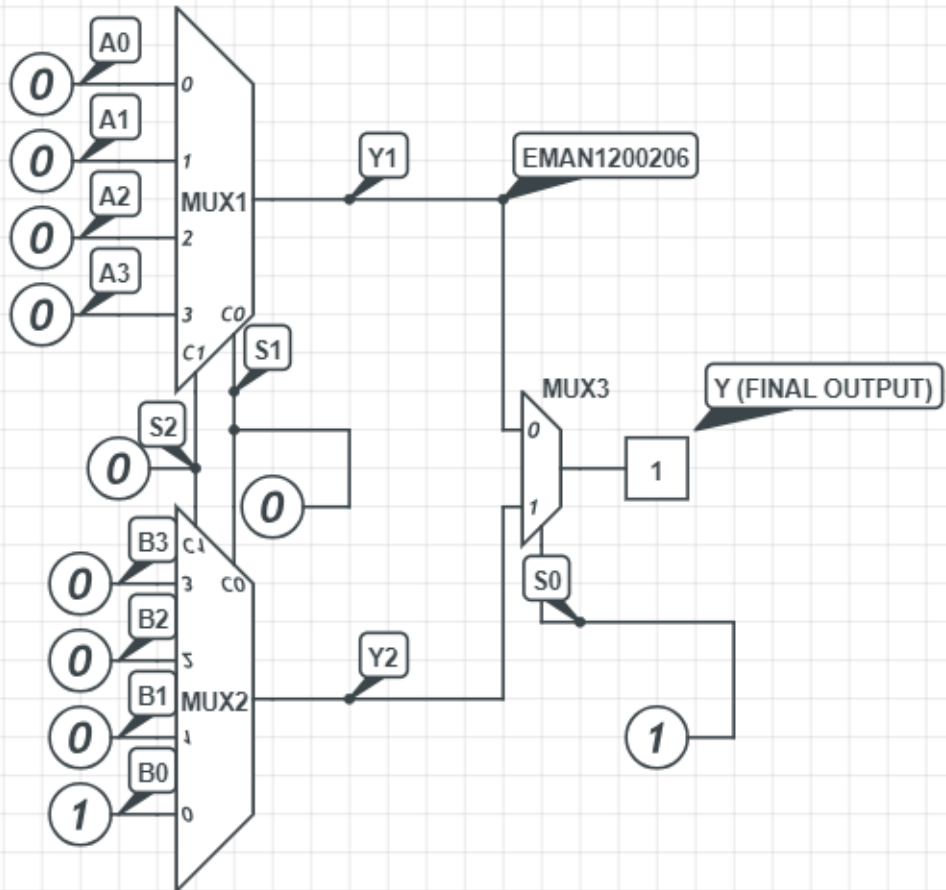


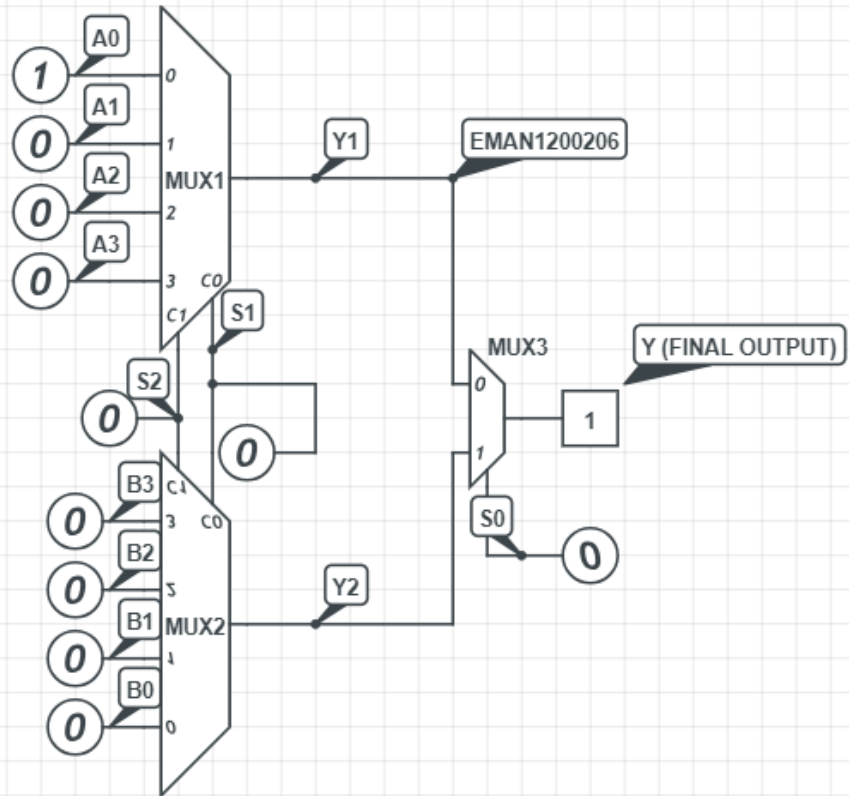

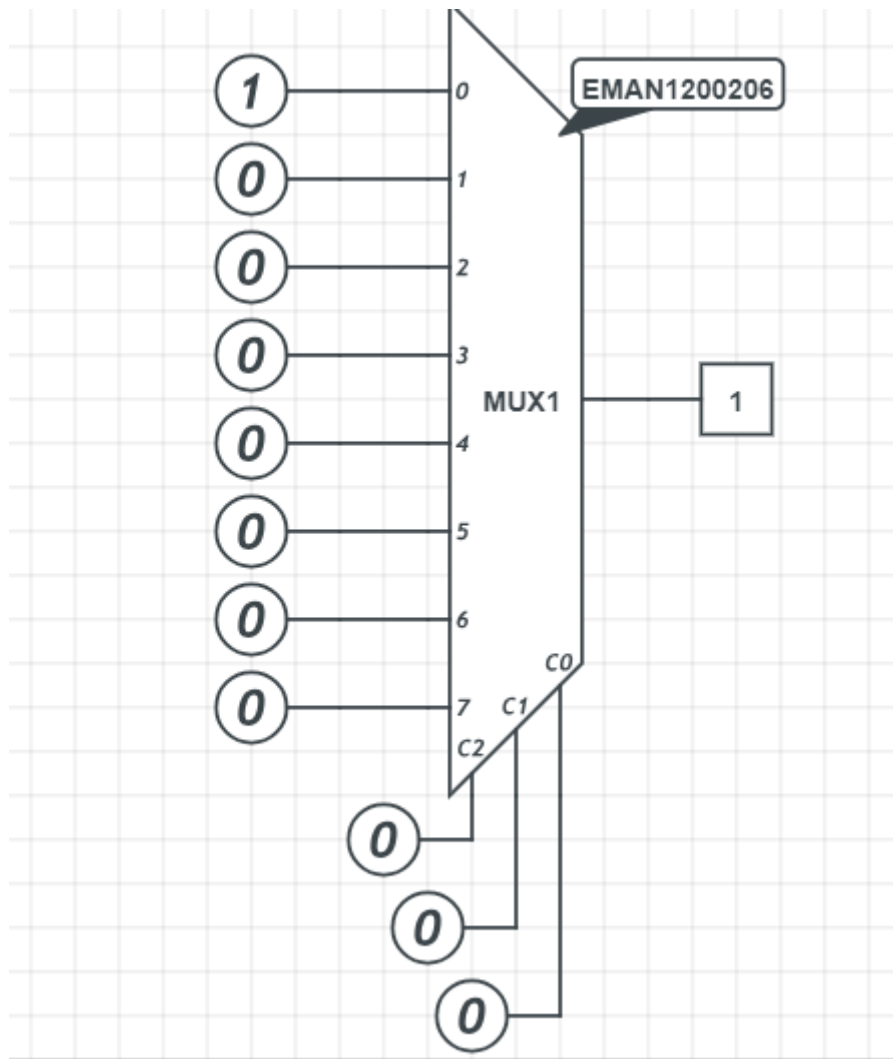


Selection Inputs			Output
S ₂	S ₁	S ₀	Y
0	0	0	I ₀
0	0	1	I ₁
0	1	0	I ₂
0	1	1	I ₃
1	0	0	I ₄
1	0	1	I ₅
1	1	0	I ₆

1	1	1	I_7
---	---	---	-------

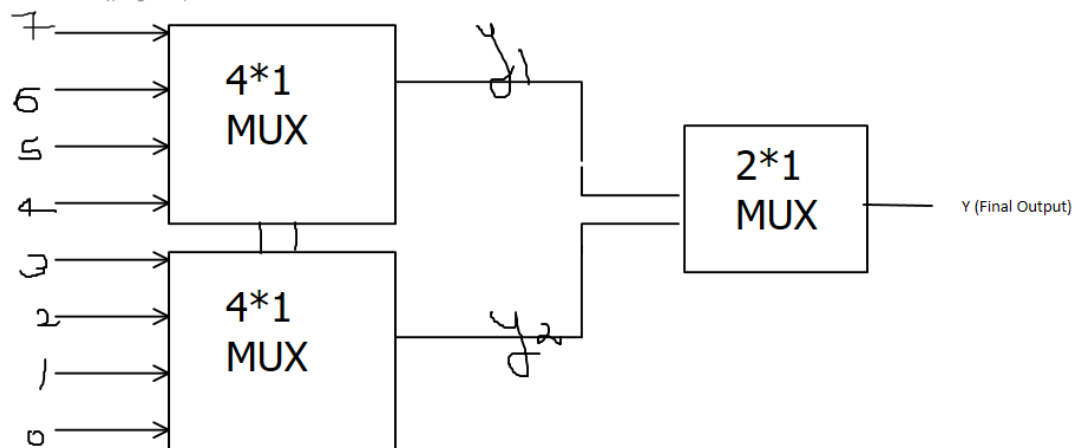

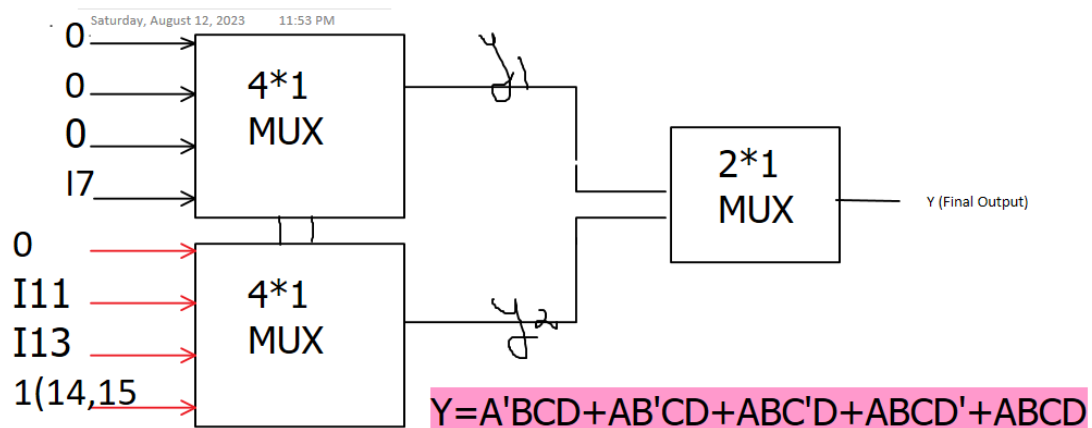2. Design a Majority Circuit; a circuit that takes 4 inputs A, B, C, D, and 1 output Y. Its output equals 1 when 3 or 4 of the inputs are 1. You can only use two 4x1 multiplexers.



Inputs				Output
A	B	C	D	Y
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	0

7
11
13
14
15

