



Faculty of Engineering and Technology

Department of Electrical and Computer Engineering

DIGITAL ELECTRONICS AND COMPUTER  
ORGANIZATION LABORATORY (ENCS2110)

**“Post-Lab1”**

---

Prepared by:

Name: Eman Asfour

Number: 1200206

Instructor: Dr. Jamal Seyam

Section: 4

Date: 8 / 9 / 2023


• Draw the logic diagram showing the implementation of the following Boolean equation using “NAND” gates

a)  $F = AB(CA)$ .

b)  $F = (D.A) + (C.B)$


c)  $F = XZ + Y'Z + X'YZ$

a)

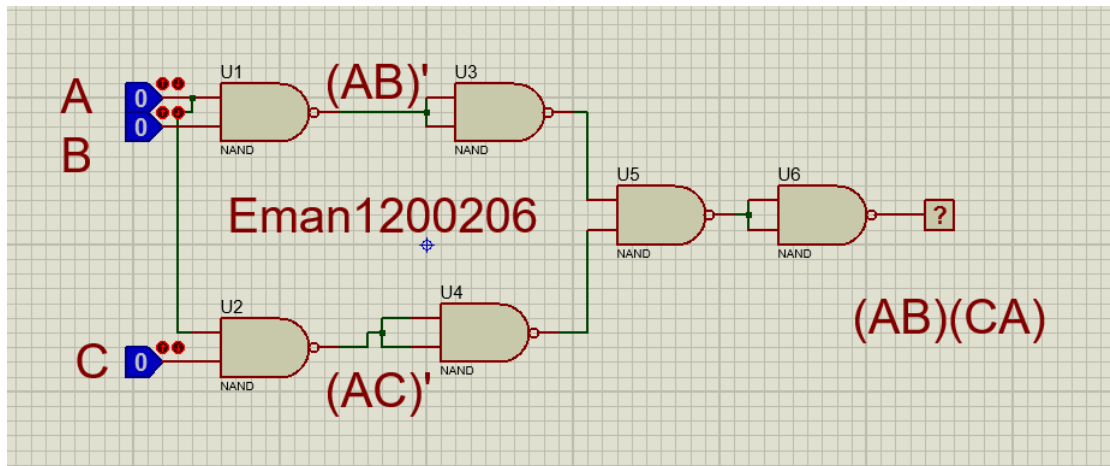

$$F = AB(CA)$$

b)

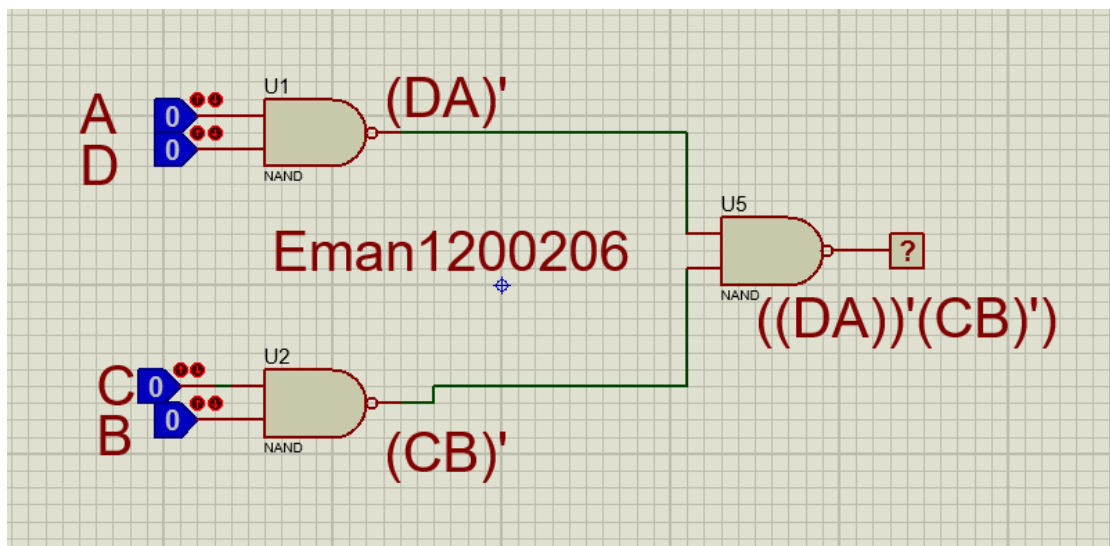


$$F = (DA) + (CB)$$

$$F' = ((DA) + (CB))' = (DA)' \cdot (CB)'$$

$$F'' = ((DA)' \cdot (CB)')'$$

c)

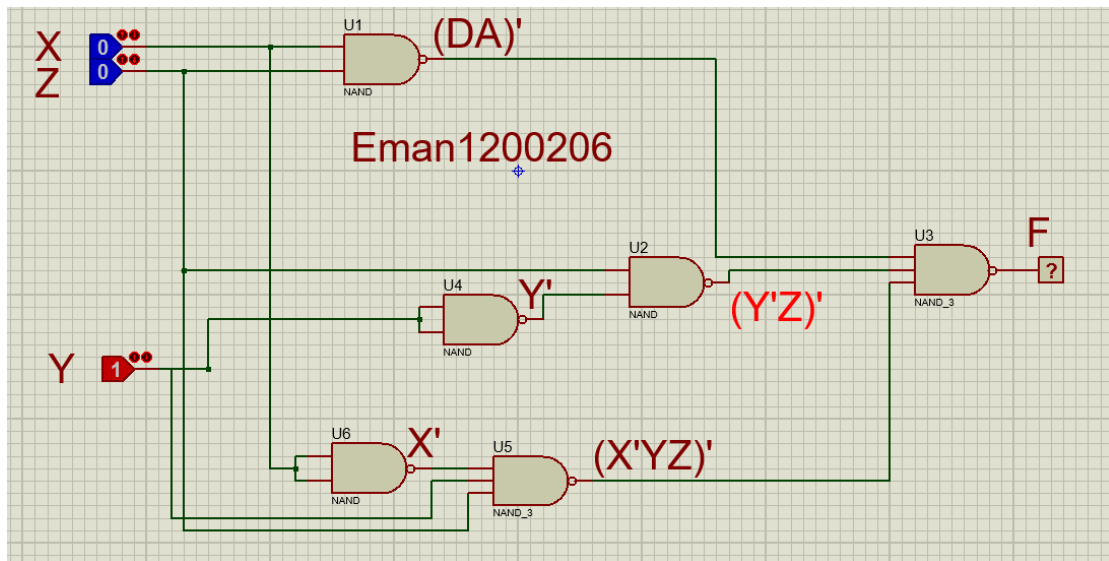


$$F = XZ + Y'Z + X'YZ$$

$$F' = (XZ)' \cdot (Y'Z)' \cdot (X'YZ)'$$

$$F'' = ((XZ)' \cdot (Y'Z)' \cdot (X'YZ'))'$$

• Draw the logic diagram of the following Boolean equations using NOR gates.

a)  $F = (A+B) (CD+A)$

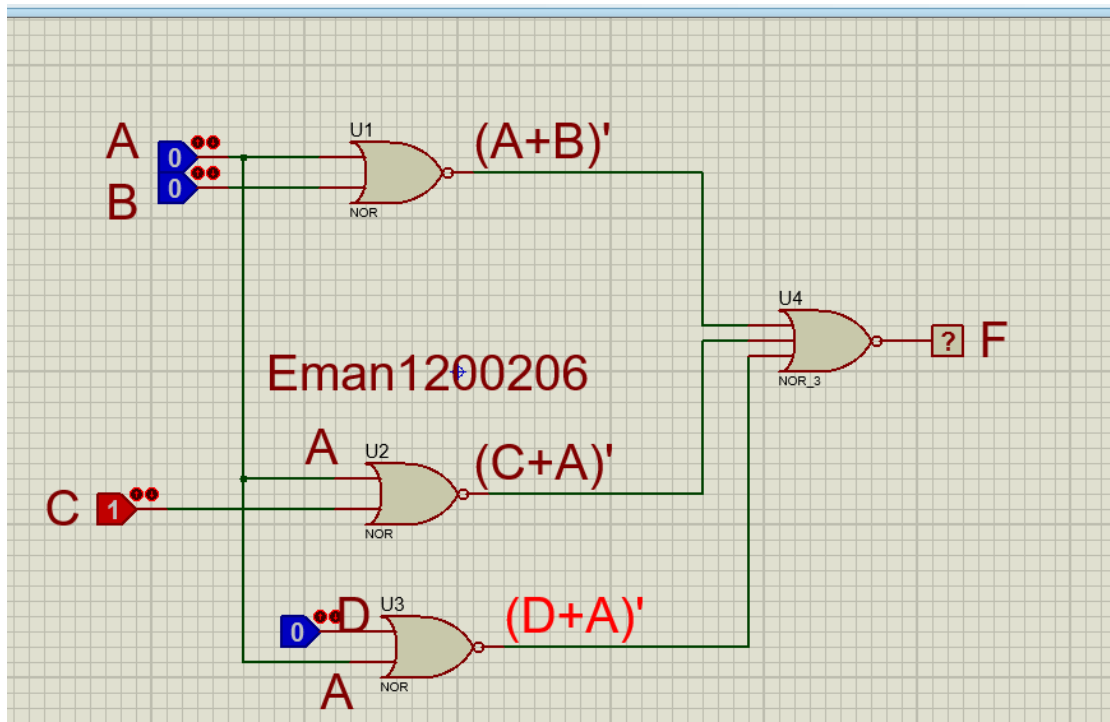


$$F = (A + B)(CD + A)$$


$$F = (A + B)(C + A)(D + A)$$

$$F' = ((A + B)' + (C + A)' + (D + A)')'$$

b)  $F = (ABC + D)C$

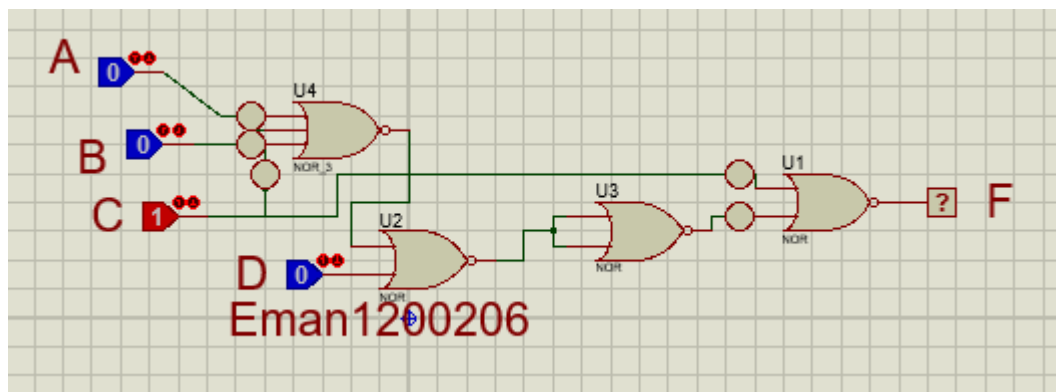

c)  $F = (X+Z) (Y'+Z) (X'+Y+Z)$

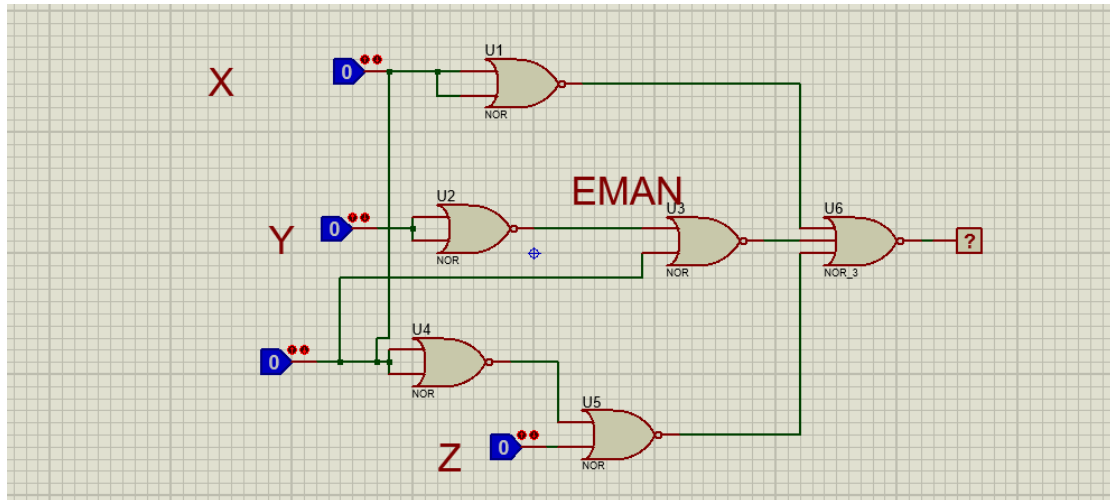


$$F = (X + Z)(Y' + Z)(X' + Y + Z)$$


$$F' = (X + Z)' + (Y' + Z)' + (X' + Y + Z)'$$

$$F'' = ((X + Z)' + (Y' + Z)' + (X' + Y + Z'))'$$

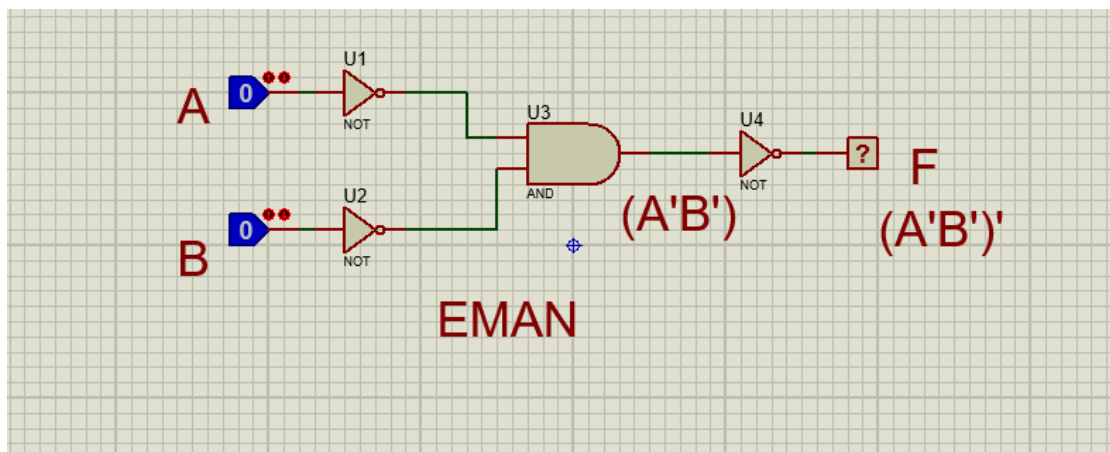**Implement the OR operation using AND, NOT gate. Draw the logic diagram and write the Boolean equation**



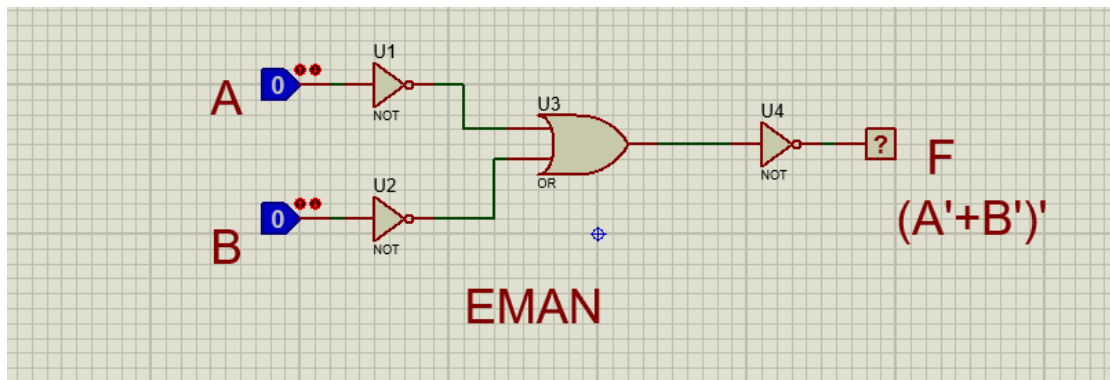**Implement the AND gate using OR, NOT gate. Draw the logic diagram and write the Boolean equation.**



**Prove that the equality operation  $F1 = AB + A'B'$  is the inverse of exclusive OR operation  $F2 = AB' + A'B$  (use Demerger's theorem).**


$$F1 = AB + A'B'$$

$$F1' = (AB + A'B')'$$

$$F1' = (A' + B')(A + B) = (A'A) + (A'B) + (B'A) + (B'B) = (A'B) + (AB') = F2$$

• Show how is it possible to reduce Boolean expressions using the Karnaugh map:

a)  $F1 = A'B'C + ABC' + A'BC' + AB'C$

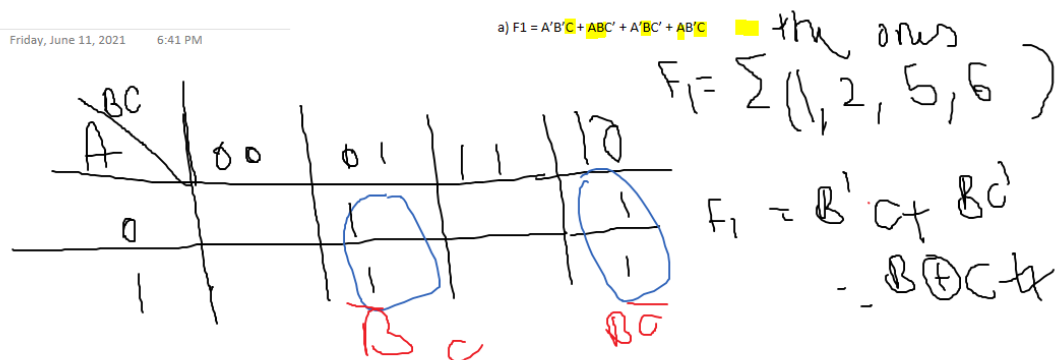

b)  $F2 = A'D + A'C + BD + AB'D'$

Tuesday, August 8, 2023 11:47 PM

b)  $F_2 = A'D + A'C + BD + AB'D'$   
 $= A'B'CD + A'BC'D + A'B'CD + A'B'CD + A'B'CD + A'BCD + ABCD + AB'CD + AB'CD$   
 $= (1, 2, 3, 5, 6, 7, 8, 10, 13, 15)$   
 $F_2 = A'D + A'C + BD + AB'D'$

AB \ CD	00	01	11	10
00			1	1
01			1	1
11			1	1
10	1			1

$\overline{A}\overline{B}D'$   $\overline{A}D$   
 $\overline{A}B'D'$   $\overline{A}C$

c)  $F_3 = A'BCD + ABCD' + A'BCD' + ABCD'$

'c)  $F_3 = A'BCD + ABCD' + A'BCD' + ABCD$   
 7 14 6 8

AB \ CD	00	01	11	10
00				
01			1	1
11			1	1
10			1	1

$F = BCD' + A'BC$   
 $\Sigma (6, 7, 14)$

d)  $F_4 = A'B'C'D' + AB'CD' + A'B'CD' + A'BC'D'$

AB \ CD	00	01	11	10
00	1			1
01	1			
11				
10				1

$\overline{A}\overline{B}C'D' + \overline{A}C'D'$   
 d)  $F_4 = A'B'C'D' + AB'CD' + A'B'CD' + A'BC'D'$

$F_4 = \Sigma (0, 2, 4, 10)$

