



Faculty of Engineering and Technology

Department of Electrical and Computer Engineering

DIGITAL ELECTRONICS AND COMPUTER
ORGANIZATION LABORATORY (ENCS2110)

“Post-Lab2”

Prepared by:

Name: Eman Asfour

Number: 1200206


Instructor: Dr. Jamal Seyam


Eng. Haleema Hmedan


Section: 4

Date: 8 / 11 / 2023

1. Design an 8-bit BCD adder

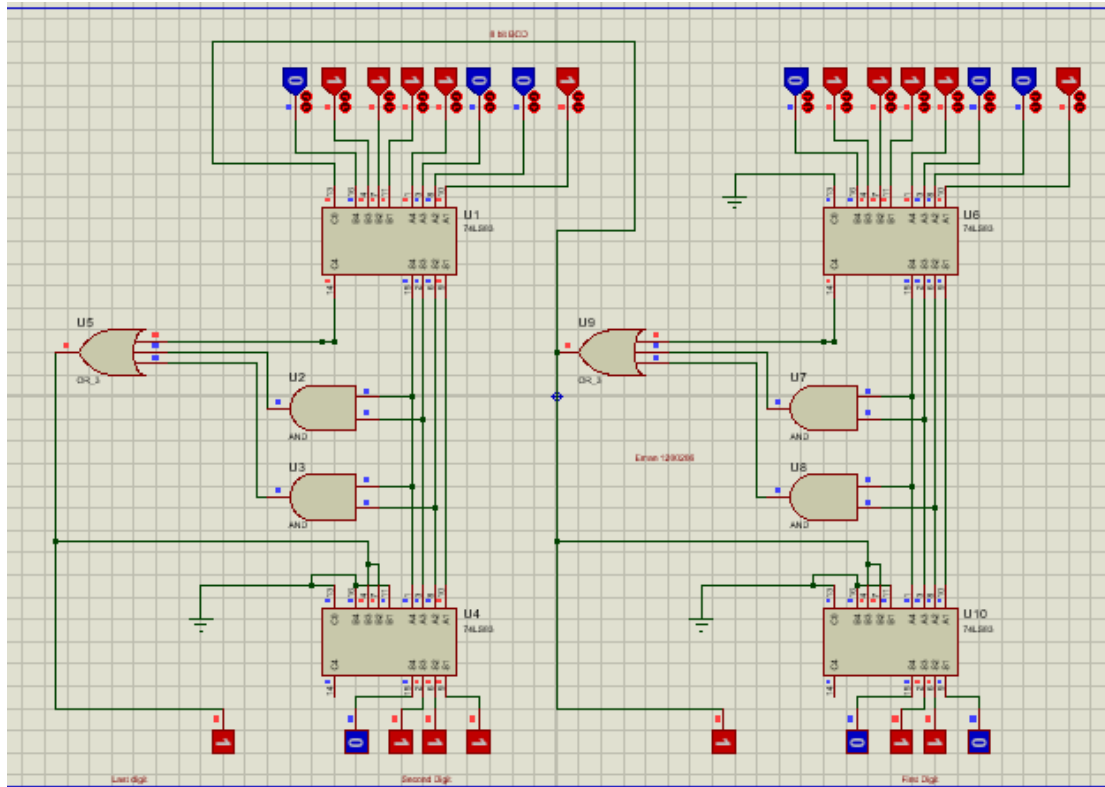

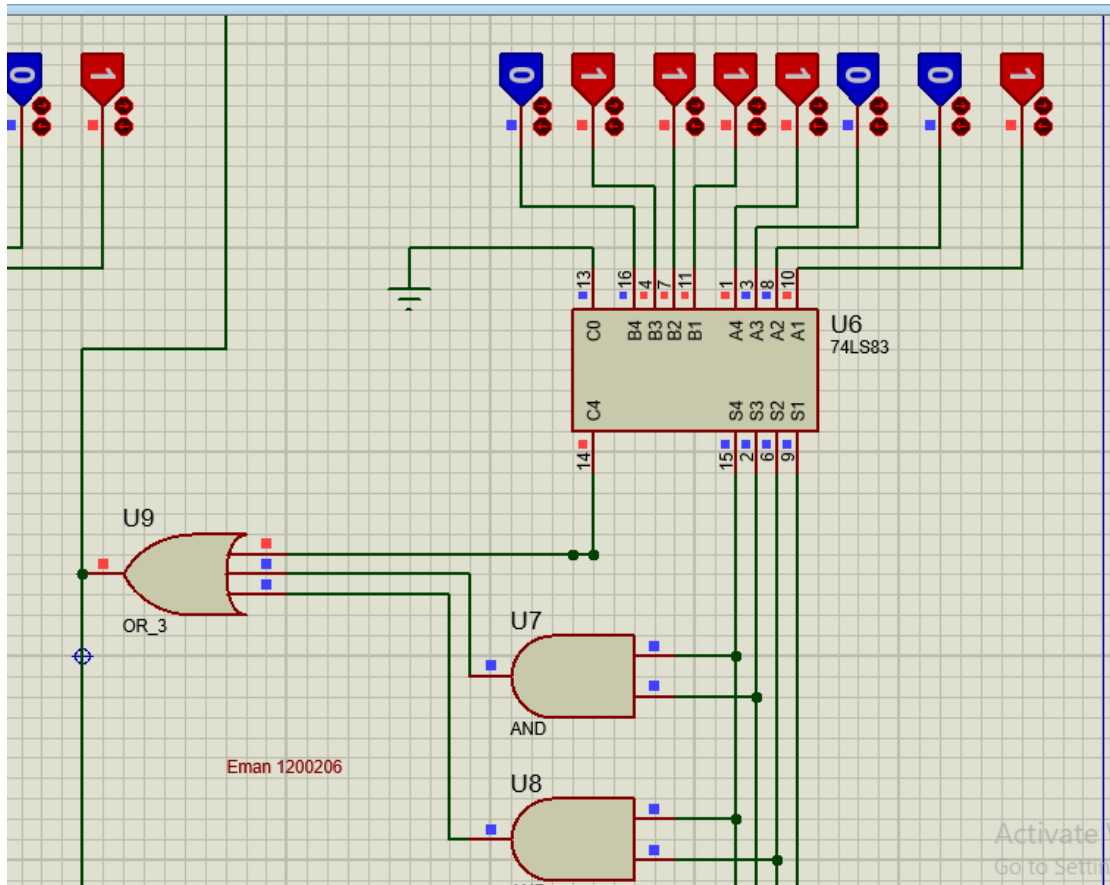

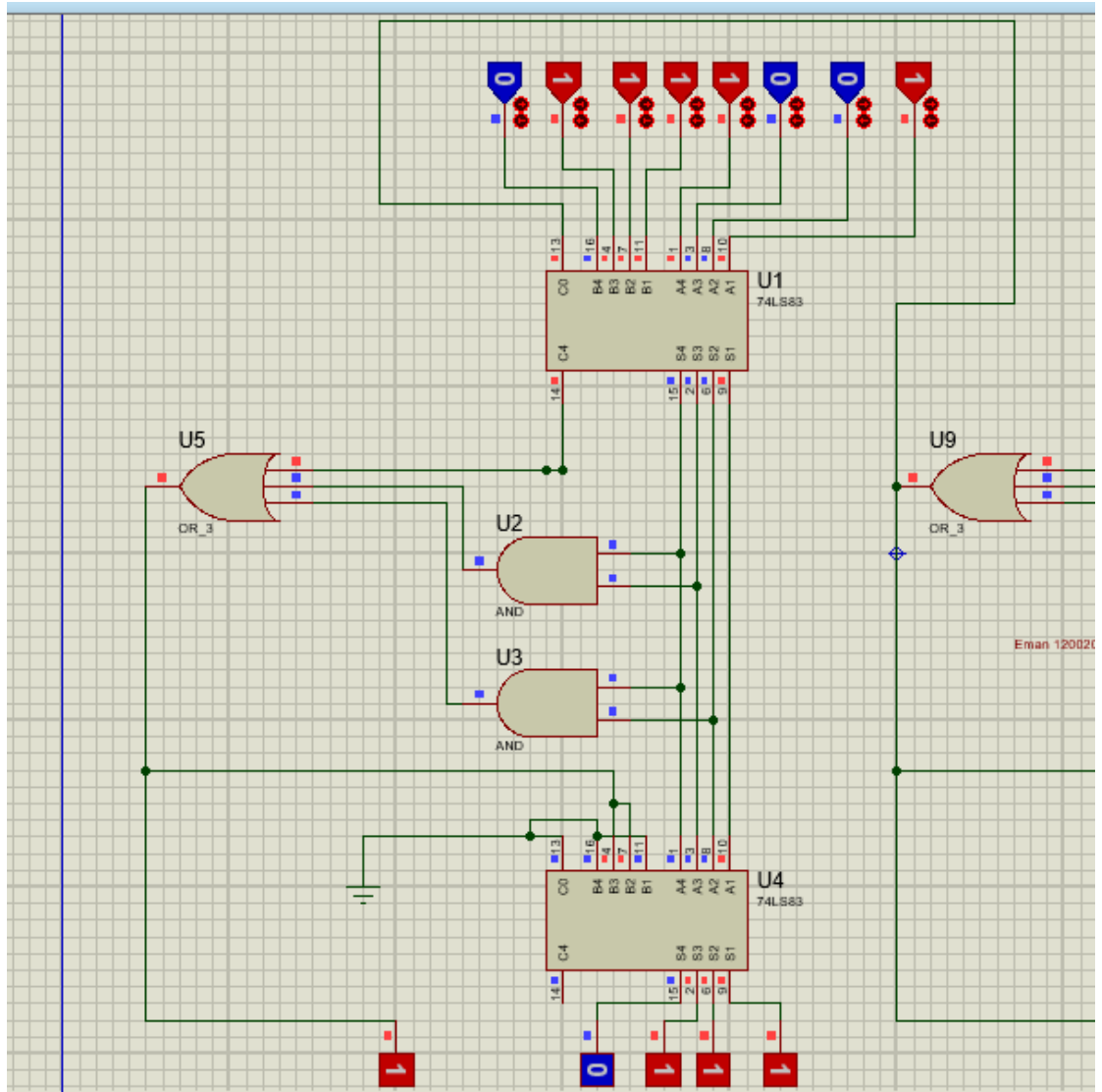



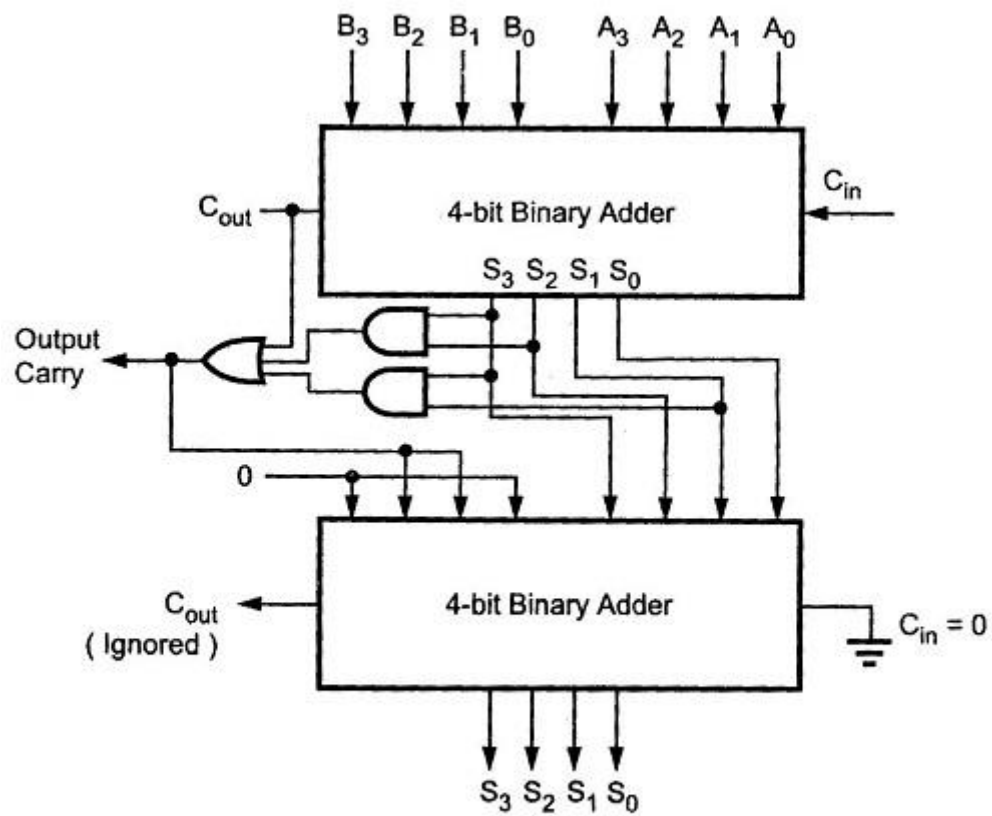
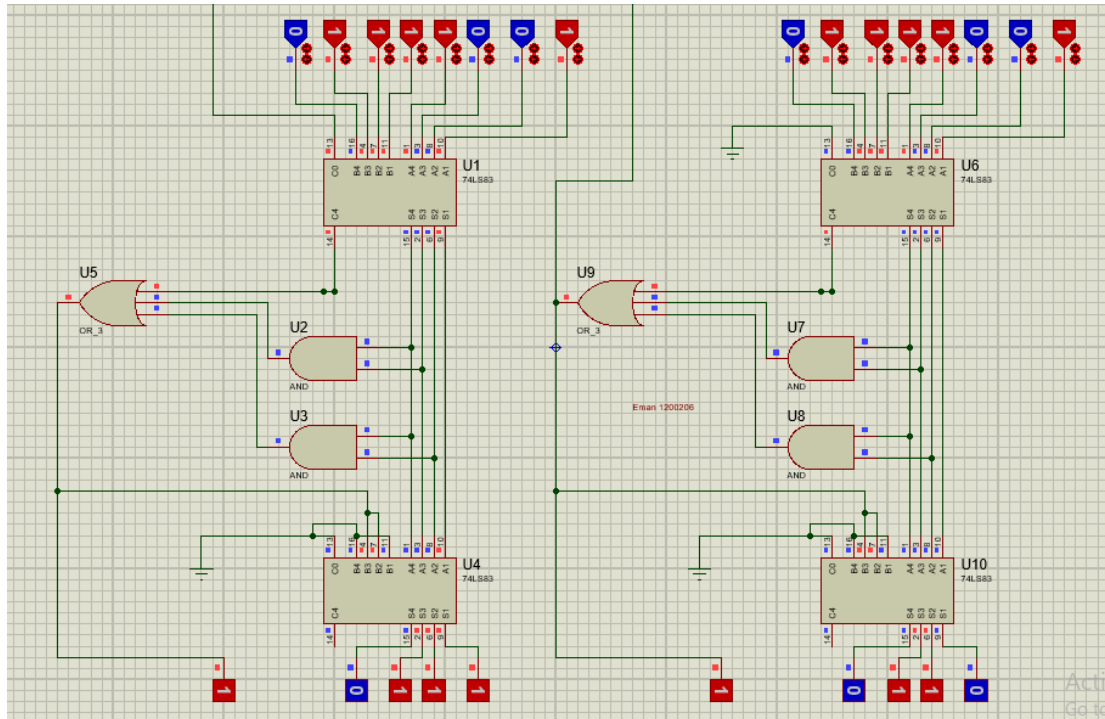
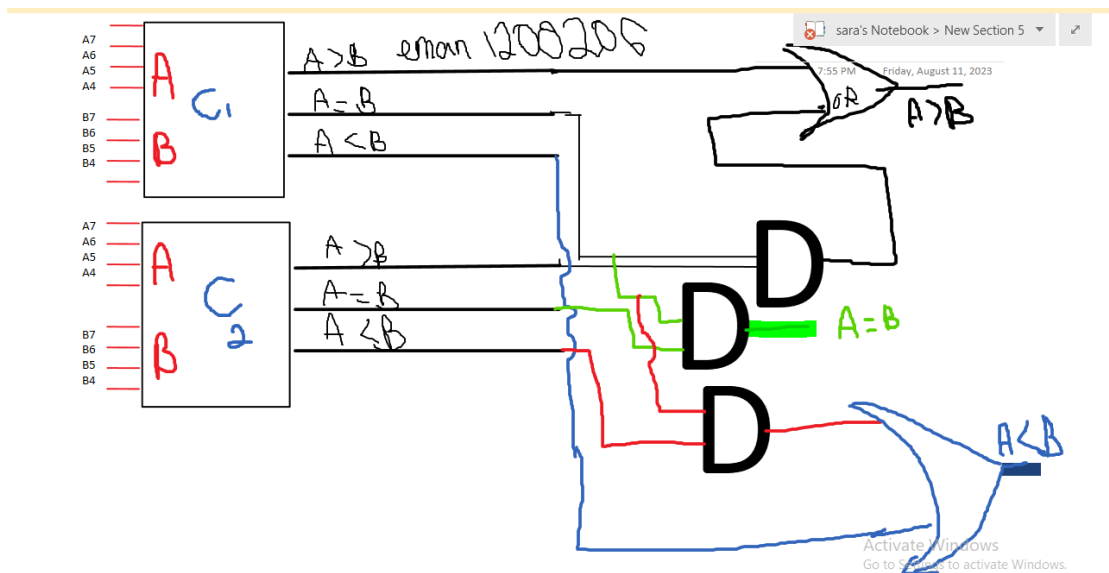
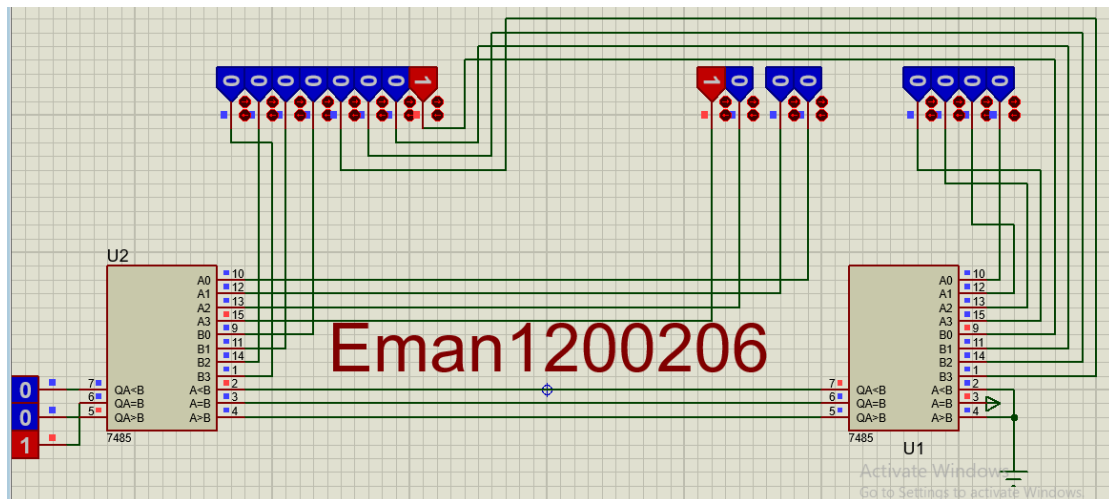




Fig. 3.32 Block diagram of BCD adder


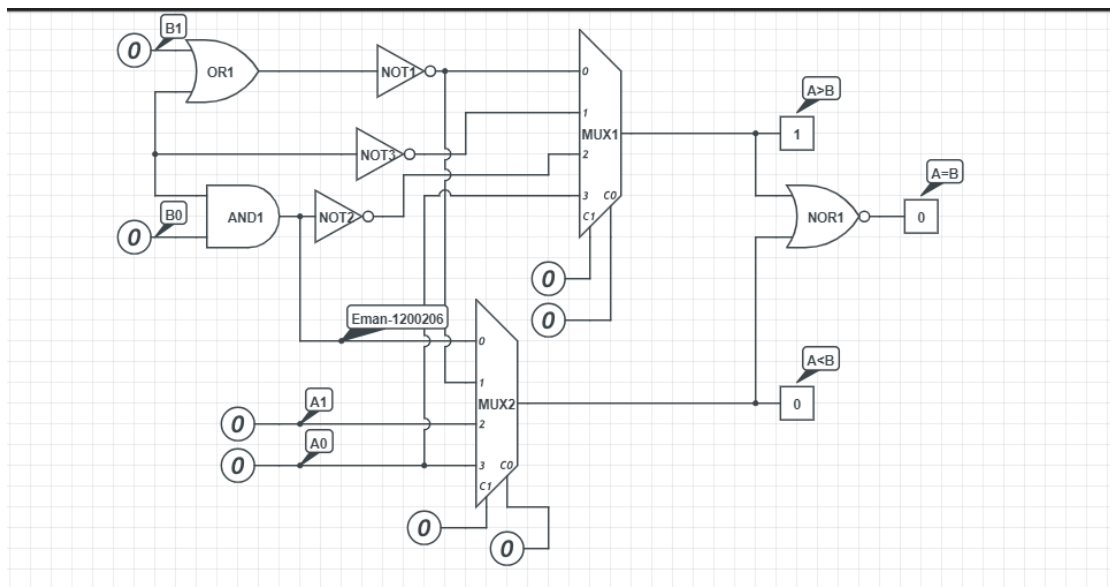
2. Design an 8-bit comparator using 2 of the 4-bit comparator.



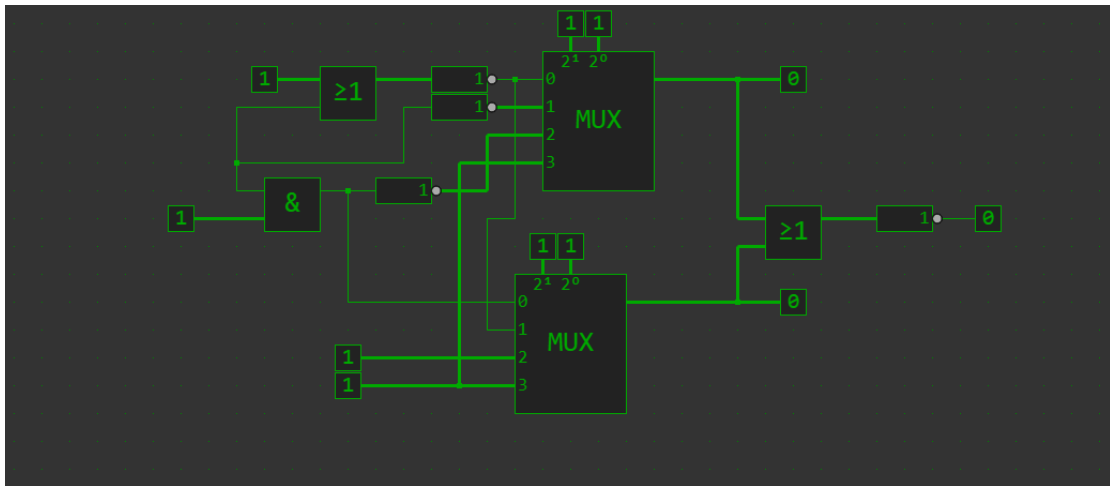3.A 4-inputs, 3-outputs circuit that compares 2-bit unsigned numbers and outputs a '1' on one of three output lines according to whether the first number is greater than, equal to, or less than the other number. You can only use two 4×1 multiplexer.



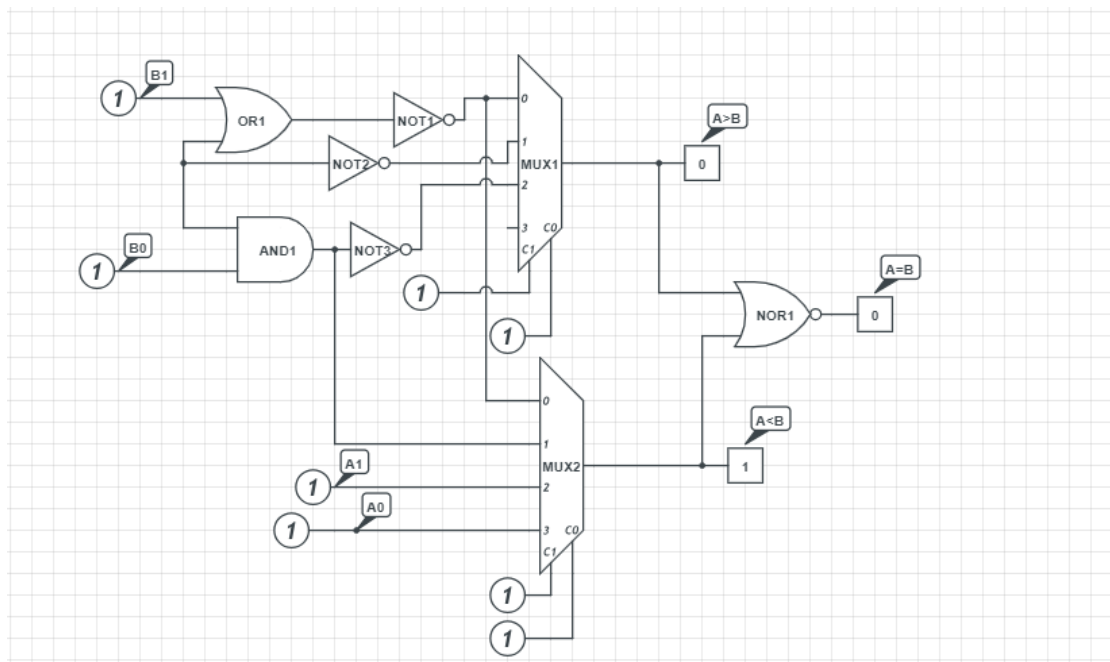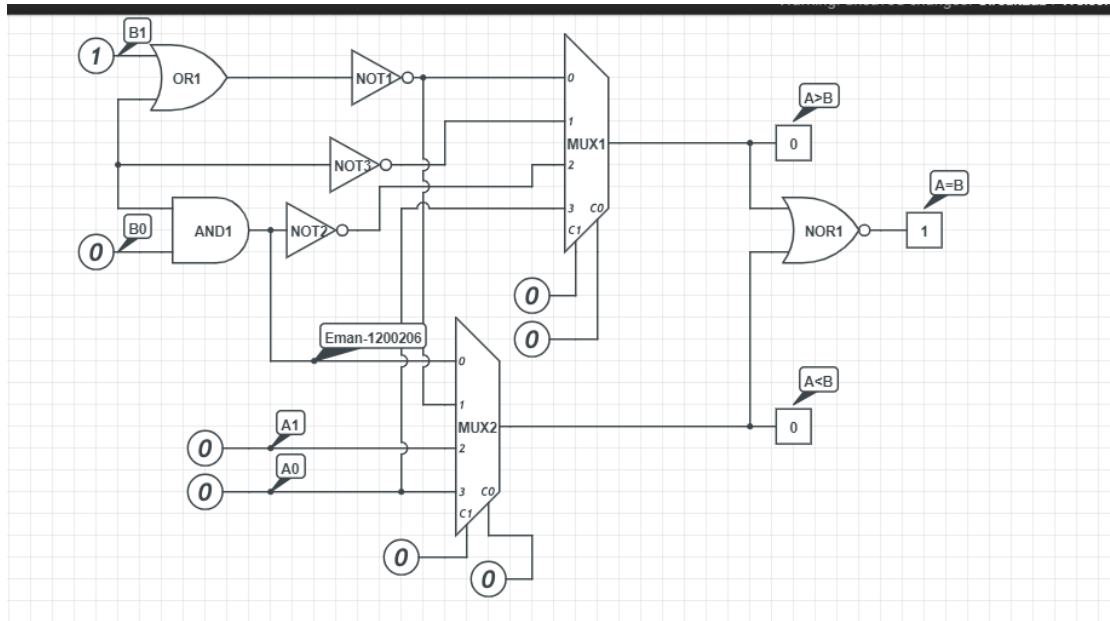

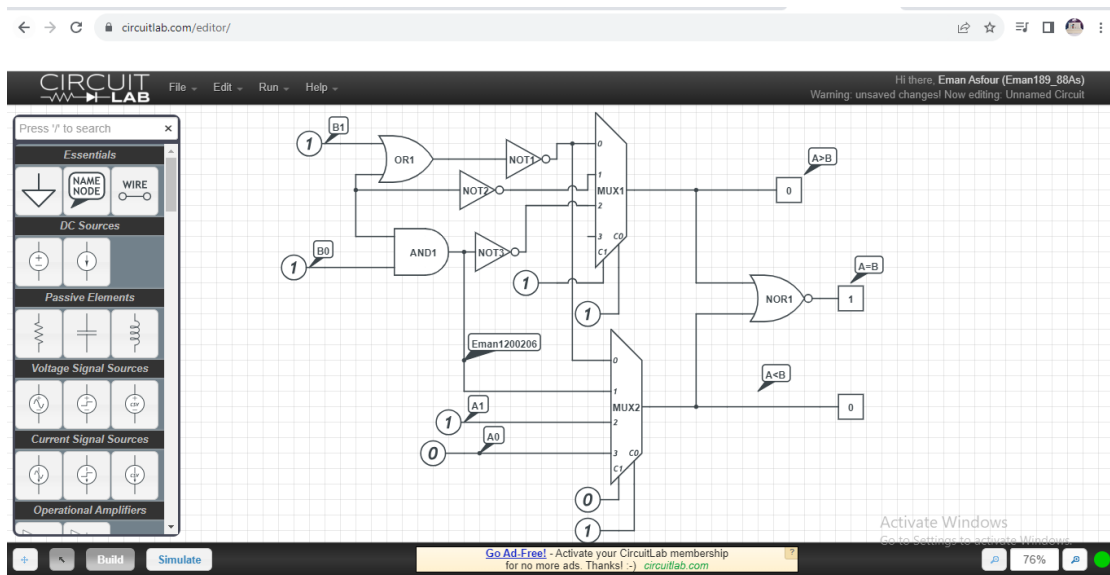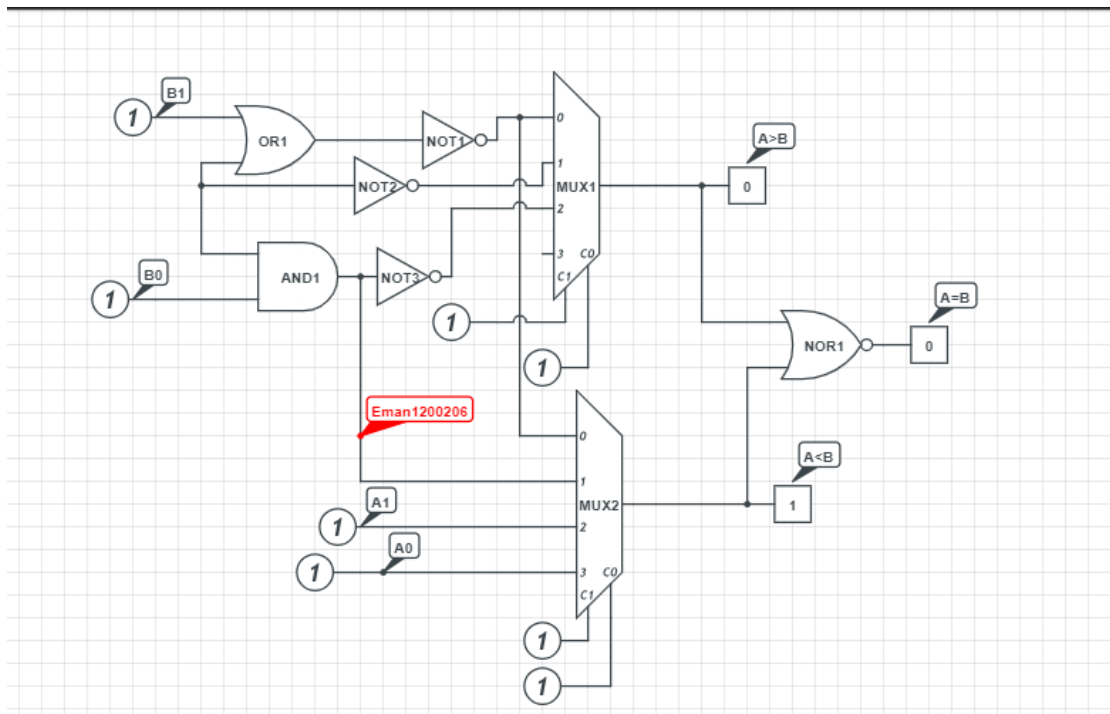

A1	A0	B1	B0	Sel1	Sel0	Sel1	Sel0	GreaterThan	EqualTo	LessThan
0	0	0	0	0	0	0	0	1	0	1
0	0	0	1	0	1	0	1	1	0	0
0	0	1	0	1	0	1	0	1	0	0
0	0	1	1	1	1	1	1	0	1	0
0	1	0	0	0	0	0	0	1	0	1
0	1	0	1	0	1	0	1	1	0	0

